

Lab 138 - Transistors and Amplifiers

Jonas Sjöberg (Högskolan i Gävle, Elektronikingenjörsprogrammet)
Esther Hedlund (Högskolan i Gävle, Elektronikingenjörsprogrammet)

Abstract

"This lab is meant to teach and show the practical use of NPN bjt amplifiers. The lab includes constructing and measuring DC circuits, calculating biasing networks, amplification, bandwidth and plotting characteristic curves of circuit parameters."

Contents

1	Ic-Uce-characteristics	2
1.1	Circuit	2
1.1.1	Fixed collector voltage	2
1.1.2	Measurements	2
1.1.3	Simulation	3
2	Quiescent conditions	5
2.1	Circuit	5
2.1.1	Curve	5
3	Uce/Ib transfer function	5
4	Ic/Ib characteristics and current amplification	5
4.1	Measurements	5
4.2	Comments	5

5	BJT biasing	7
6	BJT amplifier	8
6.0.1	Amplification	8
6.0.2	Frequency response	9
6.0.3	Improved biasing	9
6.0.4	“Noiseless” biasing	9

1 Ic-Uce-characteristics

1.1 Circuit

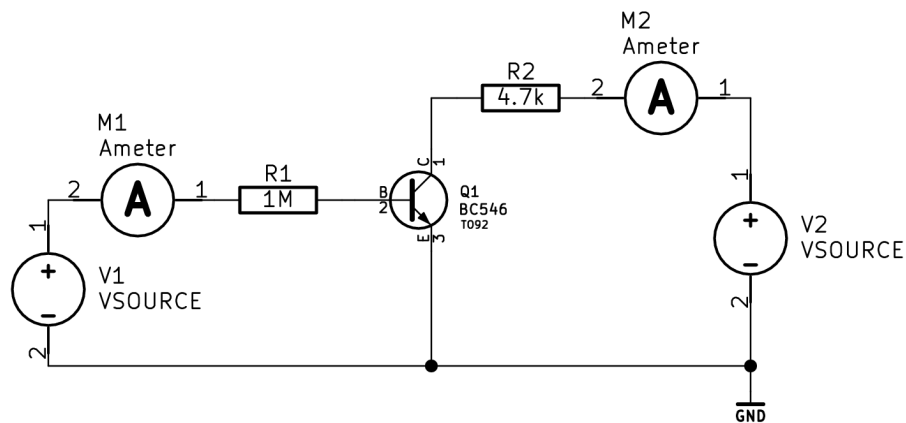


Figure 1: Measurement setup

1.1.1 Fixed collector voltage

With the collector resistor R_2 left out or shorted, an adjustable power supply is connected directly across the collector-emitter junction, fixing the collector voltage. First we get the base currents for known collector currents. Adjusting voltage V_1 translates to varying the base current I_B and in turn the collector current I_C . The transistor used is a BC547C.

1.1.2 Measurements

I_c (mA)	I_b (μ A)
0.5	1.14
1.0	2.11
1.8	3.72

Table 1: Measurement of base current vs collector current

The base current is then held at a constant value and the collector-emitter voltage is swept over a range of 0-10V in 1V steps. The results is given in the plot.

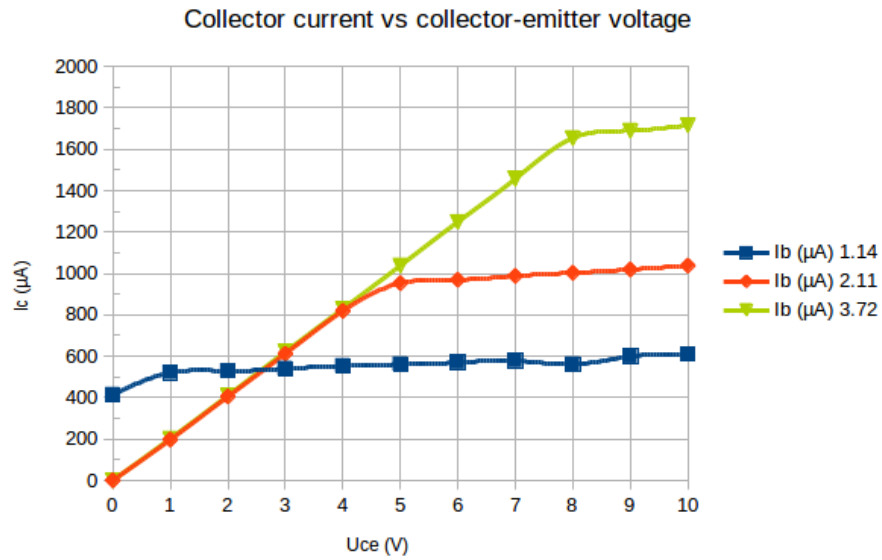


Figure 2: I_c - U_{ce} results

1.1.3 Simulation

Spice circuit simulation confirms that measurements reflect typical bjt characteristics. The program used is Linear Technology ltspice, models extracted from transistor datasheet parameters.

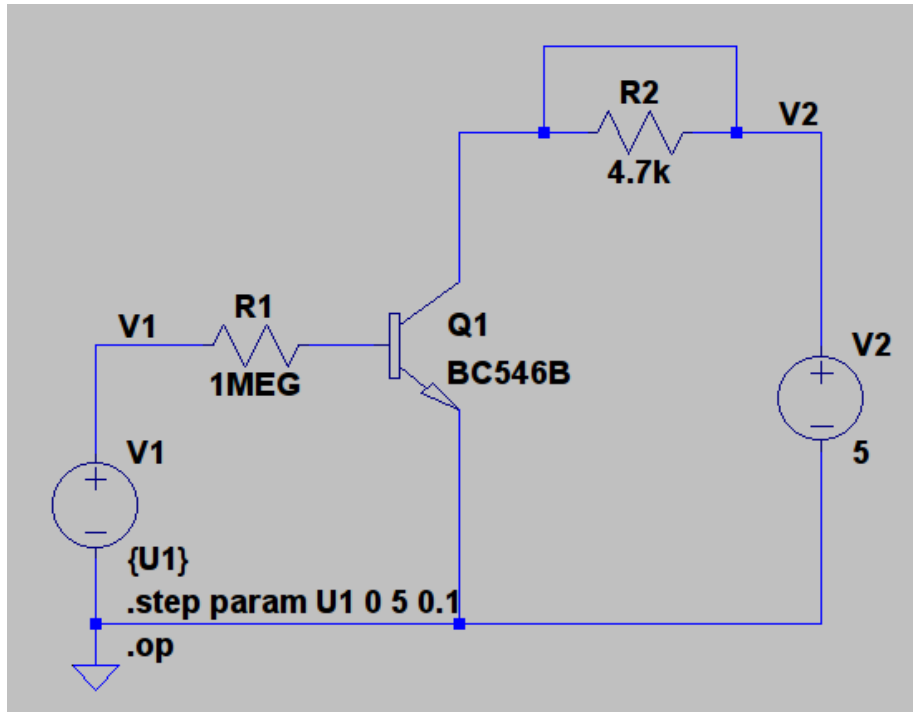


Figure 3: Ltpice schematic

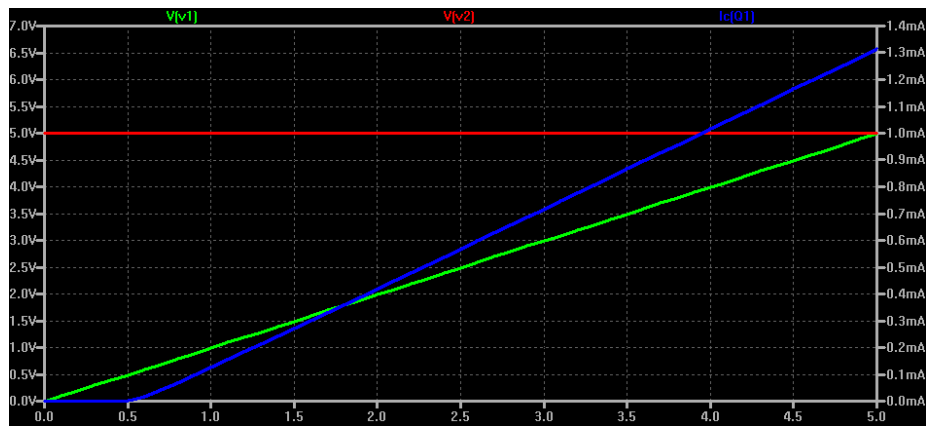


Figure 4: Ltpice simulation of Ic-Uce-characteristics

2 Quiescent conditions

2.1 Circuit

$E = 10V$ $R_c = 4.7k\Omega$

TODO!

Figure 5: TODO

2.1.1 Curve

TODO

3 U_{ce}/I_b transfer function

Examine the output signal of the first circuit. Determine the linearity of the output, as in the relation of U_{ce} to I_b . Uses the measurement setup and circuit shown in Figure 1.

4 I_c/I_b characteristics and current amplification

4.1 Measurements

4.2 Comments

TODO: Comment the curve, calculate current amplificationfactor $\Delta I_c / \Delta I_b$ in regions of interest.

TODO!

Figure 6: TODO

TODO!

Figure 7: I_c as a function of I_b

5 BJT biasing

Rb	Ve	Ve	Rc
390k Ω	00	00	00
470k Ω	00	00	00
560k Ω	00	00	00
680k Ω	00	00	00
820k Ω	00	00	00
1M Ω	00	00	00

Table 2: Bias resistor with bias voltages

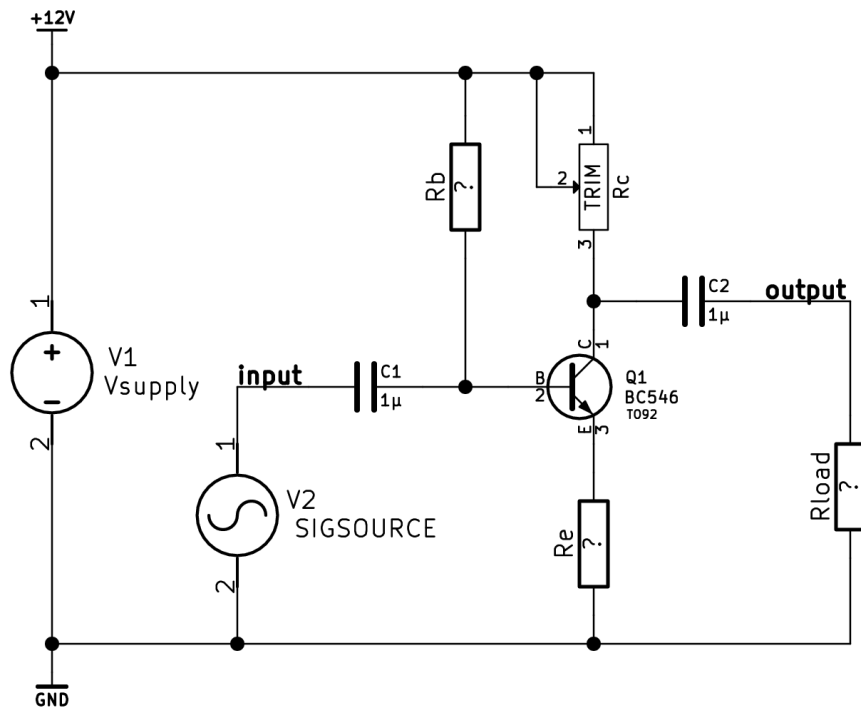


Figure 8: BJT biasing circuit

6 BJT amplifier

6.0.1 Amplification

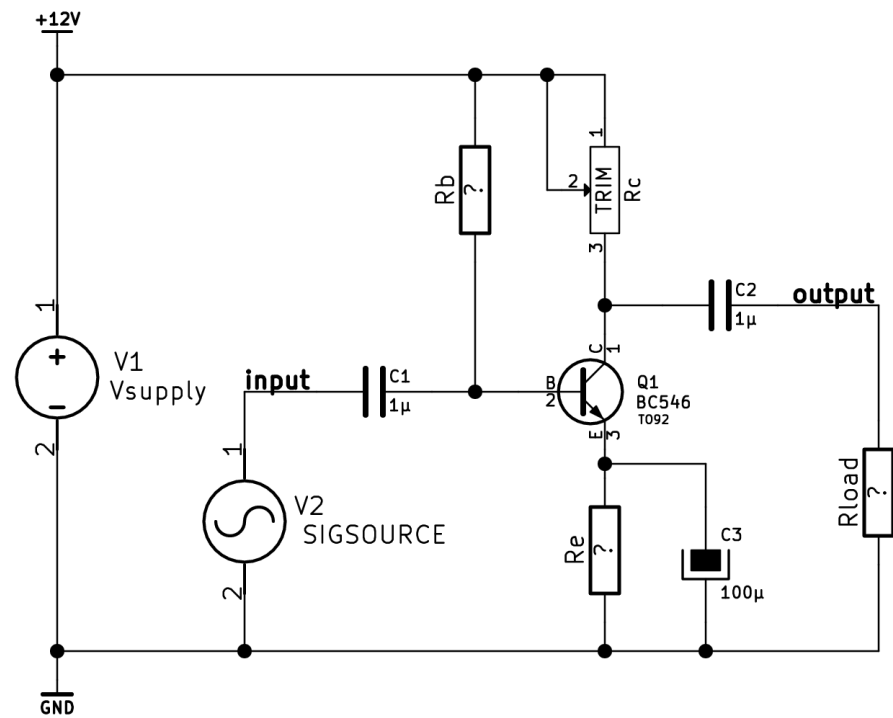


Figure 9: AC bypassed BJT amplifier

	Without AC bypass	AC bypassed
Input voltage (mVtt)	111	111
Output voltage (Vtt)	111	111
Voltage gain (multiple)	111	111
Voltage gain (dB)	111	111
Phase shift (degrees)	111	111

Table 3: Amplifier gain measurements

6.0.2 Frequency response

6.0.3 Improved biasing

The one resistor base bias is in practice not very reliable as it is dependant on transistor beta. A more practical design that scales better for production adds a second resistor, forming a voltage divider that fixes the base at a suitable level. For maximum dynamic range half of V_{supply} , plus a diode drop to compensate for the base-emitter voltage.

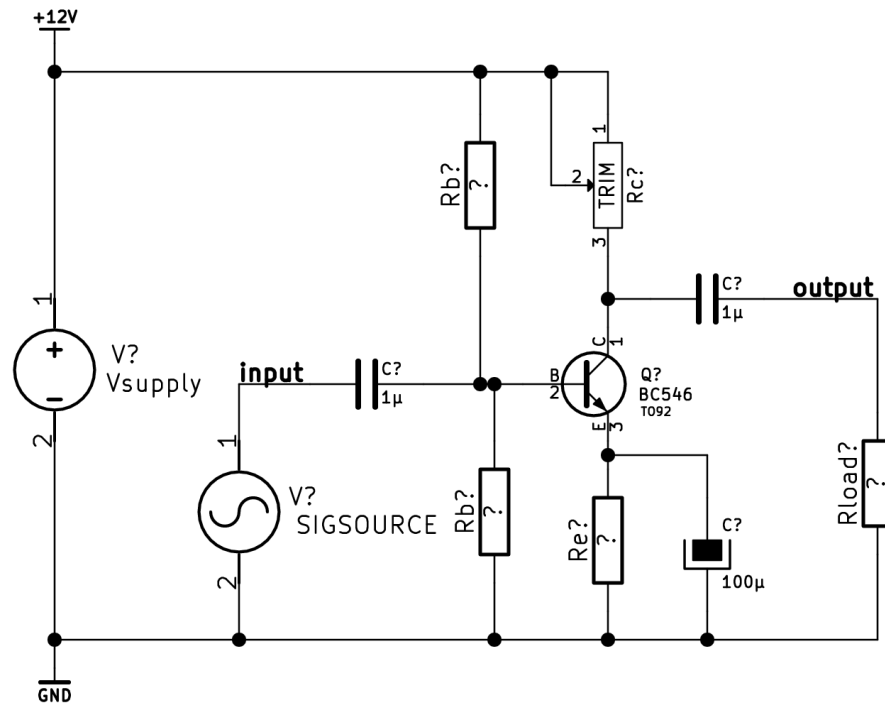


Figure 10: Voltage divider bias

6.0.4 “Noiseless” biasing

For small signals and high input impedance, the biasing can be improved further in terms of bias voltage “stiffness” and power supply noise rejection. The bias voltage is derived from a separate low impedance voltage divider, heavily filtered and almost a short circuit as far as AC signals are concerned. The bias voltage is tapped with a higher value resistor which effectively sets the input impedance of the stage.

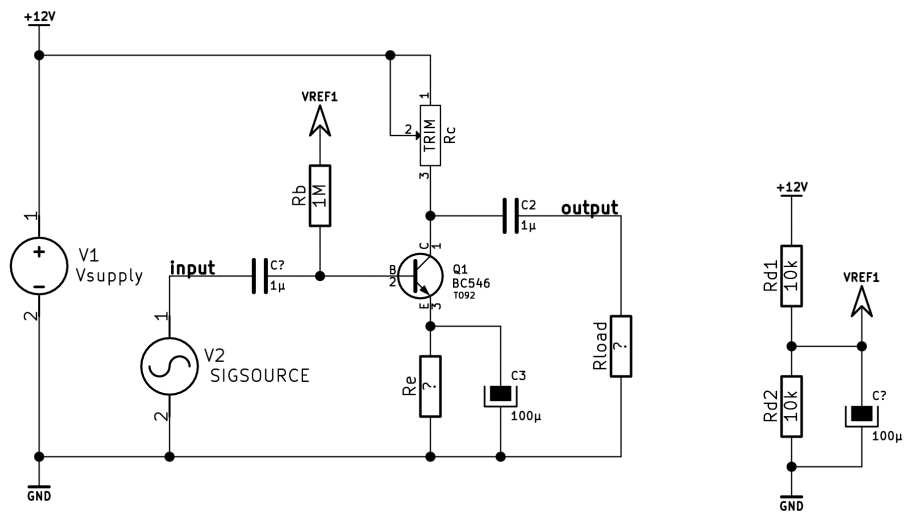


Figure 11: Voltage divider with filtered voltage reference