

Lab 138 - Transistors and Amplifiers

27 November 2014

Contents

| | | |
|----------|--|----------|
| 1 | Ic-Uce-characteristics | 2 |
| 1.1 | Circuit | 2 |
| 1.1.1 | Fixed collector voltage | 2 |
| 1.1.2 | Measurements | 2 |
| 1.1.3 | Simulation | 3 |
| 2 | Quiescent conditions | 3 |
| 2.1 | Circuit | 3 |
| 2.1.1 | Curve | 3 |
| 3 | Uce-Ib transfer function | 5 |
| 4 | Ic-Ib-characteristics and current amplification | 5 |
| 4.1 | Measurements | 5 |
| 4.2 | Comments | 5 |
| 5 | BJT biasing | 6 |
| 6 | BJT amplifier | 7 |
| 6.0.1 | Amplification | 7 |
| 6.0.2 | Frequency response | 7 |
| 6.0.3 | Improved biasing | 7 |
| 6.0.4 | “Noiseless” biasing | 8 |

1 Ic-Uce-characteristics

1.1 Circuit

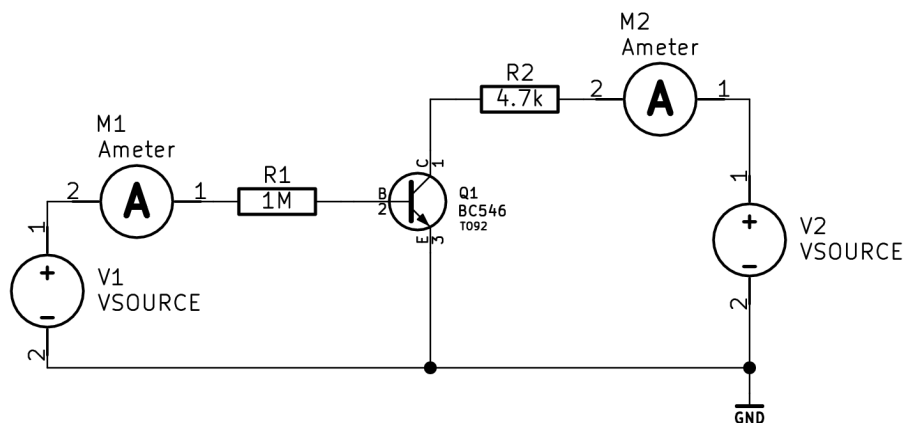


Figure 1: Measurement setup

1.1.1 Fixed collector voltage

With the collector resistor R2 left out or shorted, an adjustable power supply is connected directly across the collector-emitter junction, fixing the collector voltage. First we get the base currents for known collector currents. Adjusting voltage V1 translates to varying the base current I_b and in turn the collector current I_c . The transistor used is a BC547C.

1.1.2 Measurements

| I_c (mA) | I_b (μ A) |
|------------|------------------|
| 0.5 | 1.14 |
| 1.0 | 2.11 |
| 1.8 | 3.72 |

Table 1: Measurement of base current vs collector current

The base current is then held at a constant value and the collector-emitter voltage is swept over a range of 0-10V in 1V steps. The results is given in the

plot.

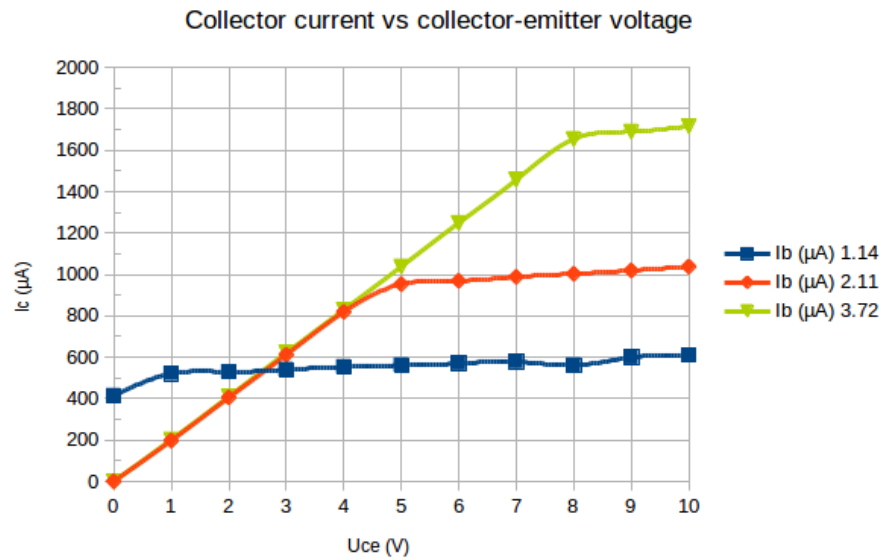


Figure 2: I_c - U_{ce} results

1.1.3 Simulation

Spice circuit simulation confirms that measurements reflect typical bjt characteristics. The program used is Linear Technology ltspice, models extracted from transistor datasheet parameters.

2 Quiescent conditions

2.1 Circuit

$E = 10V$ $R_c = 4.7k$

2.1.1 Curve

TODO

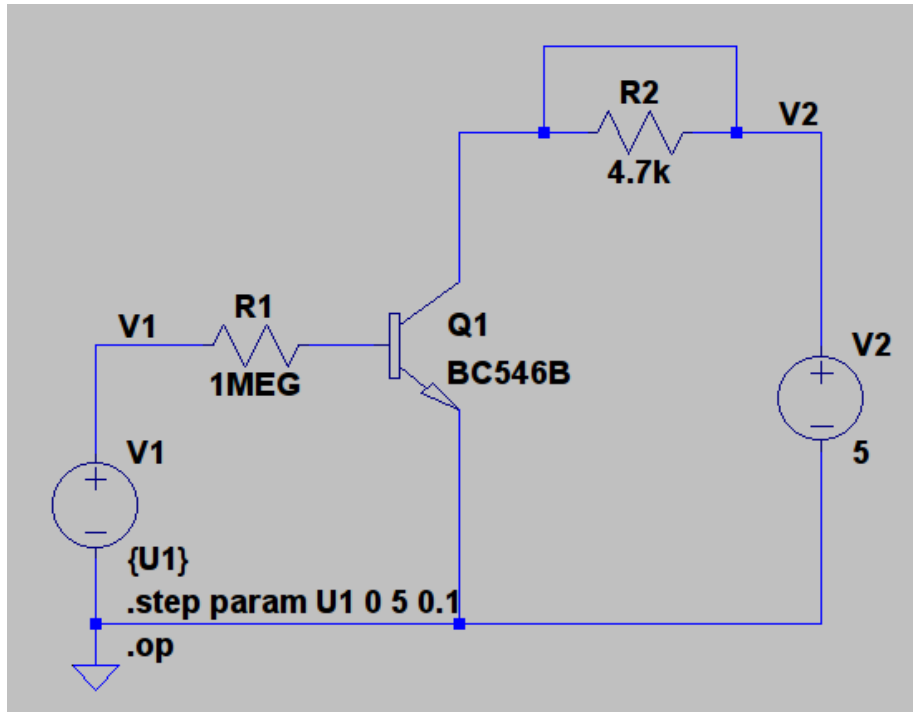


Figure 3: Ltpice schematic

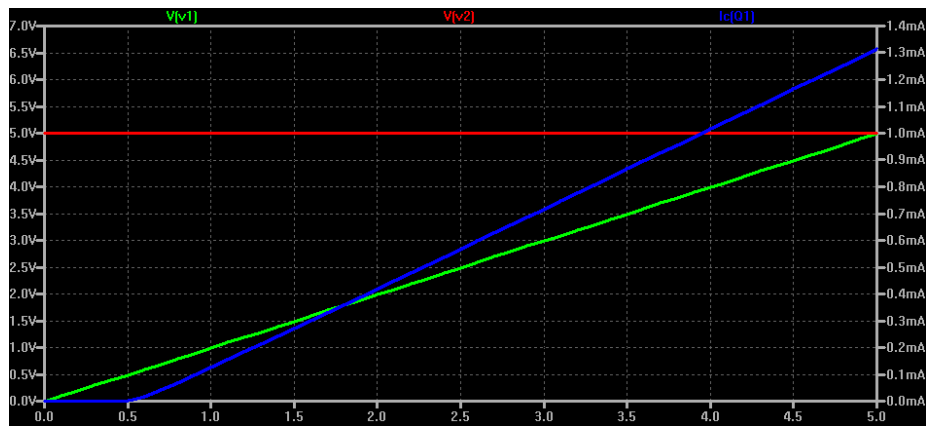


Figure 4: Ltpice simulation of Ic-Uce-characteristics



Figure 5: TODO

3 Uce-Ib transfer function

Examine the output signal of the first circuit. Determine the linearity of the output, as in the relation of Uce to Ib.

TODO



Figure 6: TODO

4 Ic-Ib-characteristics and current amplification

4.1 Measurements

4.2 Comments

TODO: Comment the curve, calculate current amplificationfactor $\Delta I_c / \Delta I_b$ in regions of interest.

TODO!

Figure 7: I_c as a function of I_b

5 BJT biasing

| R_b | V_e | V_e | R_c |
|--------------|-------|-------|-------|
| $390k\Omega$ | 00 | 00 | 00 |
| $470k\Omega$ | 00 | 00 | 00 |
| $560k\Omega$ | 00 | 00 | 00 |
| $680k\Omega$ | 00 | 00 | 00 |
| $820k\Omega$ | 00 | 00 | 00 |
| $1M\Omega$ | 00 | 00 | 00 |

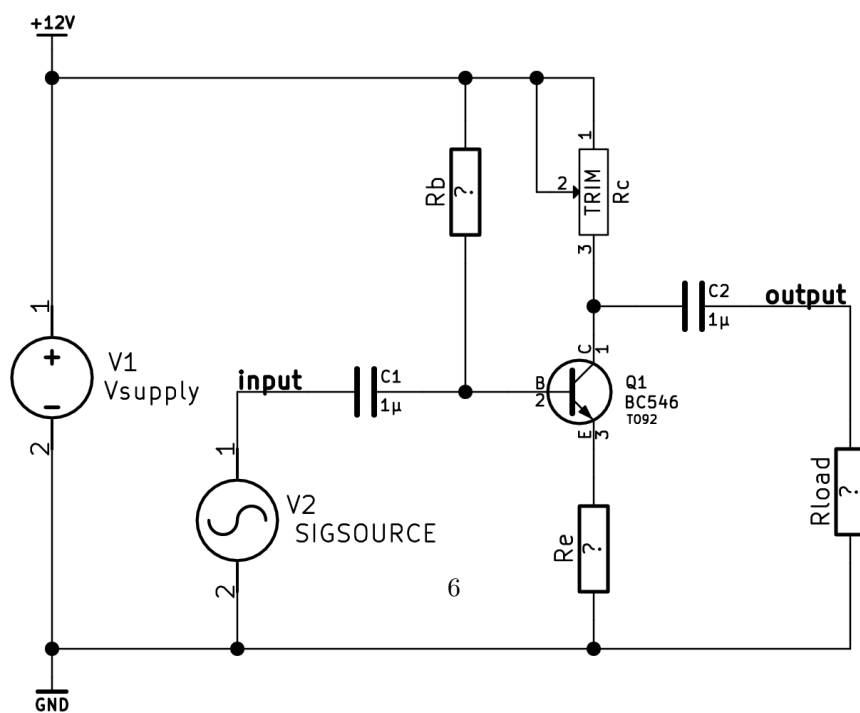


Figure 8: BJT biasing circuit

6 BJT amplifier

6.0.1 Amplification

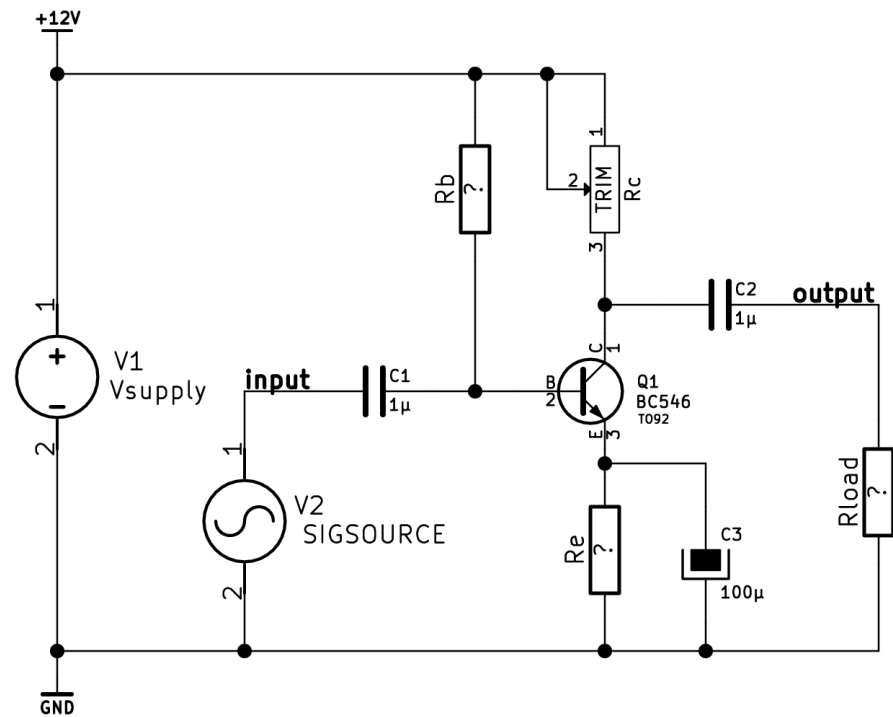


Figure 9: AC bypassed BJT amplifier

| Without AC bypass | AC bypassed |
|---------------------------------|-------------------------------|
| Input voltage (mVtt) 111 111 | Output voltage (Vtt) 111 111 |
| Voltage gain (multiple) 111 111 | Voltage gain (dB) 111 111 |
| | Phase shift (degrees) 111 111 |

Table: Amplifier gain measurements

6.0.2 Frequency response

6.0.3 Improved biasing

The one resistor base bias is in practice not very reliable as it is dependant on transistor beta. A more practical design that scales better for production adds

a second resistor, forming a voltage divider that fixes the base at a suitable level. For maximum dynamic range half of V_{supply} , plus a diode drop to compensate for the base-emitter voltage.

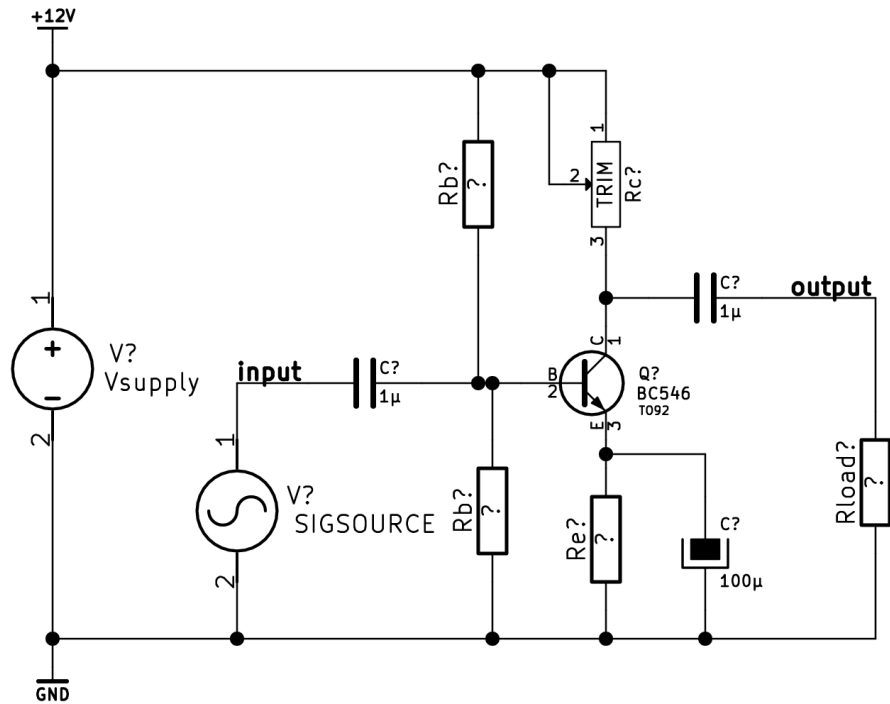


Figure 10: Voltage divider bias

6.0.4 “Noiseless” biasing

For small signals and high input impedance, the biasing can be improved further in terms of bias voltage “stiffness” and power supply noise rejection.

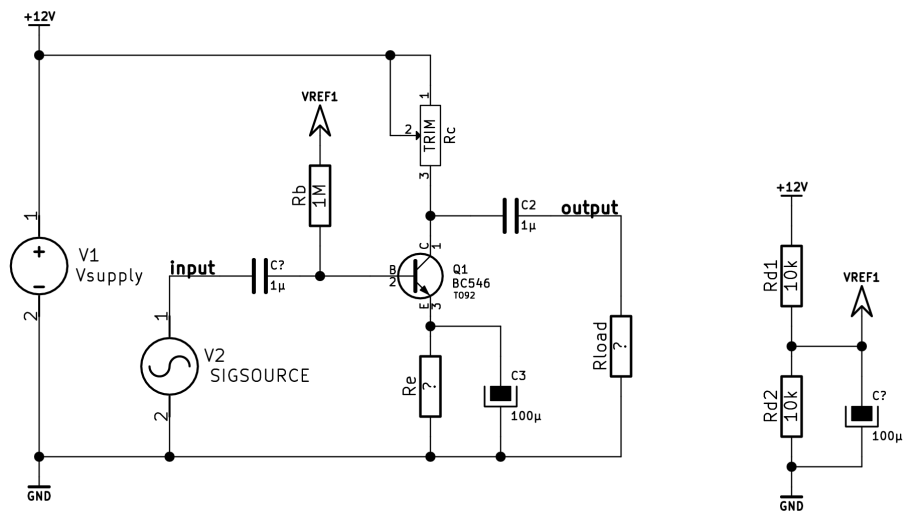


Figure 11: Voltage divider with filtered voltage reference